

Status of KUPID v2.0

2009.6.25.

Eunil Won

for Eugene Hong


(Going OSU this summer)

Korea University



History of KUPID Development

- 2006: KUPID (Korea University Preamplifier-shaper Integrated Design) ASIC fabrication thoughts - after one year successful R&D of VA-hybrid board by KU
- 2006: v1.0 submitted to Dongbu-Anam 180 nm process (a foundry in Korea)
- 2006. September: v1.0 chip received
- 2007. Jan. : we saw the first signal from KUPID v1.0
 - rather noisy, ENC~O(30,000)
 - small amplification: cannot detect one MIP from Si sensors
- 2008: v2.0 design optimized for small ENC and large gain
- 2009. May: v2.0 design submitted to IBM 130 nm process (via MOSIS) : [Belle-II note 0008 is on the web](#)

KUPID v1.0

 

Almost same
scale

  


(New PCB for better
biasing)

Now at least simulation
“agrees” with data !

: due to

- Cable capacitance inclusion
- Availability of Spectre transient response

 Basic structure: a preamplifier-shaper chain



A simplified view of (typical) preamplifier-shaper chain design.

- preamplifier: pMOS based folded-cascode structure with current sources
- shaper: typical CR-RC filtering

Note: no sample-hold, no MUX in v2.0

Noise sources from amplifiers

- Transistor **1/f noise** (carrier trap in semiconductor), transistor **channel noise**, and **Bulk-resistance noise** (white thermal noise) are main sources of noise
- Noise of a charge amplification electronics is expressed in equivalent noise charge (ENC)

$$\text{ENC}/C_{\text{det}} = \frac{e}{q} \left[\frac{A_1}{WL} + \frac{A_2 kT}{g_m T_p} + \frac{A_3 kT}{T_p} \right]^{\frac{1}{2}}$$

From Nygard
Nucl. Instr. Meth.
A 301, 506 (1991).

A_i : constants g_m : transconductance T_p : output peak time $e = 2.718$

Key point to reduce ENC : control W, L and g_m of input transistor

Noise sources from amplifiers

- In strong inversion region,

$$g_m \propto \sqrt{\frac{W}{L} I_D}$$

I_D : transistor drain current

- As a result, usually we make input transistor with small L and long W

Operating region and W/L of input transistor

- There are three operating regions for FET, weak inversion, strong inversion, and velocity saturation region.
- For each region, different optimized value for input transistor gate capacitance

From Connor Nucl. Instr. Meth.A 480, 713 (2002).

$$\frac{C_{\text{det}}}{I_D} < \frac{6\mu}{v_{\text{sat}}^2}$$


velocity saturation

$$\frac{6\mu}{v_{\text{sat}}^2} < \frac{C_{\text{det}}}{I_D} < \frac{3L_{\text{min}}^2}{2\mu(nV_t)^2}$$

strong inversion

$$\frac{3L_{\text{min}}^2}{2\mu(nV_t)^2} < \frac{C_{\text{det}}}{I_D}$$

weak-strong
boundary

 

Operating region and W/L of input transistor

- With drain current 200 μA , 20 pF detector capacitance, our system is operating in Weak-strong Inversion boundary
- In this case, optimized value for input transistor gate capacitance is

$$C_{g,opt} = \frac{L_{min}^2}{2\mu(nV_t)^2} I_D = 1.1 \text{ pF}$$

From Connor Nucl.
Instr. Meth.A 480, 713
(2002).


Decision of operating region and W/L of input transistor

- From simulation result, we can obtain C_{gg} (notation in SPICE)

$$C_{gg} = \frac{dQ_g}{dV_g}$$

- We obtained $C_{gg} = 1 \text{ pF}$ with $W/L = 1.5\mu\text{m}/130\text{nm}$
- We started schematic simulation for our preamplifier with this W/L value.


Schematic Drawing of preamp +shaper

 

Until now, we designed 5 different preamplifier-shaper channel.

They have different models (nfet, nfet_rf), different input transistor gate capacitance, and current source load for readout.

set4 : lowest ENC expected

 

For lowest noise, current source FETs should be small as possible as all FETs are noise source.


Current source load is attached to make simulation result same with real data (scope read).

Simulation result.

(set4 : lowest ENC expected)


Transient

Transient Response

 


AC

AC Response

 

Noise




Noise Response

 

At 10 pF detector capacitance, output signal from 1 MIP (25,000 e-) is 30.4mV with 130 ns peak time.

Simulation result.

(set4 : lowest ENC expected)

   

Gaussian shape output.
Shaper out -> low offset
Preamp out -> high offset

Shaper AC response
shows CR-RC filtering.

Simulation result.

(set4 : lowest ENC expected)

Detector Cap (pF)	Vop (mV)	RMSnoise(10k,100MHz) (V)	ENC
0	44.0	0.0002437	138.4
5	36.1	0.0003017	208.9
10	30.4	0.0003681	302.7
15	25.7	0.0004249	413.4
20	21.8	0.0004714	540.6

We think we can read output signal from 1 MIP as ENC of 302 is much less than input electrons 25,000

$$\text{input el.} : V_{op} = ENC : \text{noiseRMS}$$


$$ENC = \frac{25,000 \times \text{noiseRMS}}{V_{op}}$$

1 MIP = 25,000 electrons

However, real noise detection value (with chip) may be bigger than above.
There will be many parasitic noise sources such as detector leakage current, noise from power supply, etc.

Simulation result.

(set4 : lowest ENC expected)

 

Other designs show little more noise than this.
(ex. $ENC = 225 + 26 / pF$)

Further reduction of ENC noise

과제명: renewal schematic simulation result 과제번호: 100 2009. 5. 4.

① mimcap $\rightarrow$ w:L ratio $\Rightarrow \sim 1:1$ (case for rotation)

② shp input transistor $\rightarrow$ w/L $\Rightarrow 14\mu/130n$ (nf=7)
 $w/L = 1\mu/130n$
 (for DRC: connection with mimcap...)

③ e.t.c. $\rightarrow$ bias control combine, subc, mimcap(sub).

test3 $\rightarrow$ Set1 ~ 5

Files: /work/KUPID/MOSIS/20090504-renewal-sim-result/

Set	Configuration	V _{op} @ 10pF, 1MIP	ENC	Notes
Set1	(nfet + subc, w/L = 1.5 μ /130n)	100.7mV	177.2 + 23.8/pF	(no probe)
Set2	(nfet-rtf, w/L = 1.5 μ /130n)	105.3mV	149.1 + 22.3/pF	(no probe)
Set3	(nfet-rtf, w/L = 900 μ /130n)	109.7mV	134.9 + 23.6/pF	(no probe)
Set4	(nfet + subc + load, w/L = 1.5 μ /130n)	30mV	256.2 + 49.7/pF	(10pF, 10M Ω probe)
Set5	(nfet-rtf + load, w/L = 900 μ /130n)	76mV	99.4 + 18.2/pF	(10pF, 10M Ω probe)

Lowest until now!

증인서명
 일자
 발명자
 기록자

http://research.korea.ac.kr

Snapshot of Eugene's logbook:


Note the date (2009. May, 4) and the submission deadline is 2009. May 11

Further optimization in the shaper side parameters - simulation shows $< 100 + 18$ /pF


But: usually SPICE simulation underestimates real ENC : so don't get too excited yet

Layout design (preamp)


Set I preamplifier part
is finished.

 

Layout design for SetI (preamp + shaper)

 

Floor plan

 

Summary and plan

- KUPID 2.0 design submitted to IBM 130 nm process on May 11, 2009
- We expect improved ENC values, based on the SPICE simulation
- We expect to receive chip this summer: hardware test will be interesting
- We plan to include sample/hold, MUX at the next stage